

1. The output F of the digital circuit shown can be written in the form(s)_____

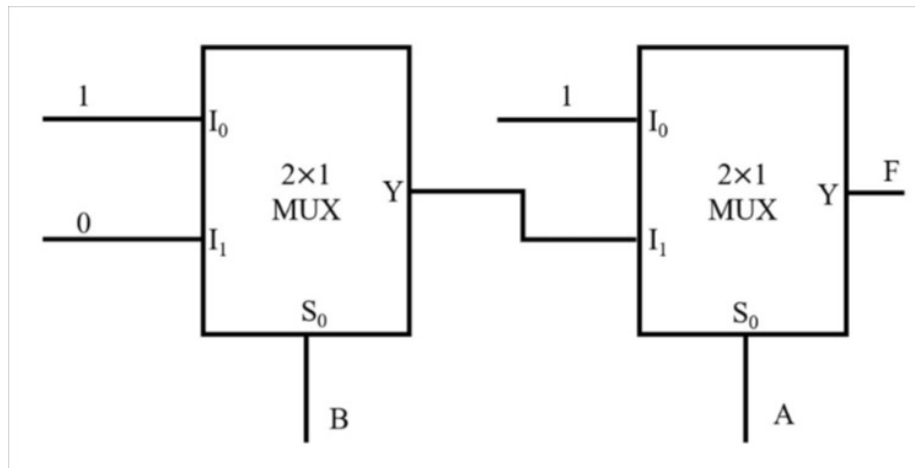


Figure 1: